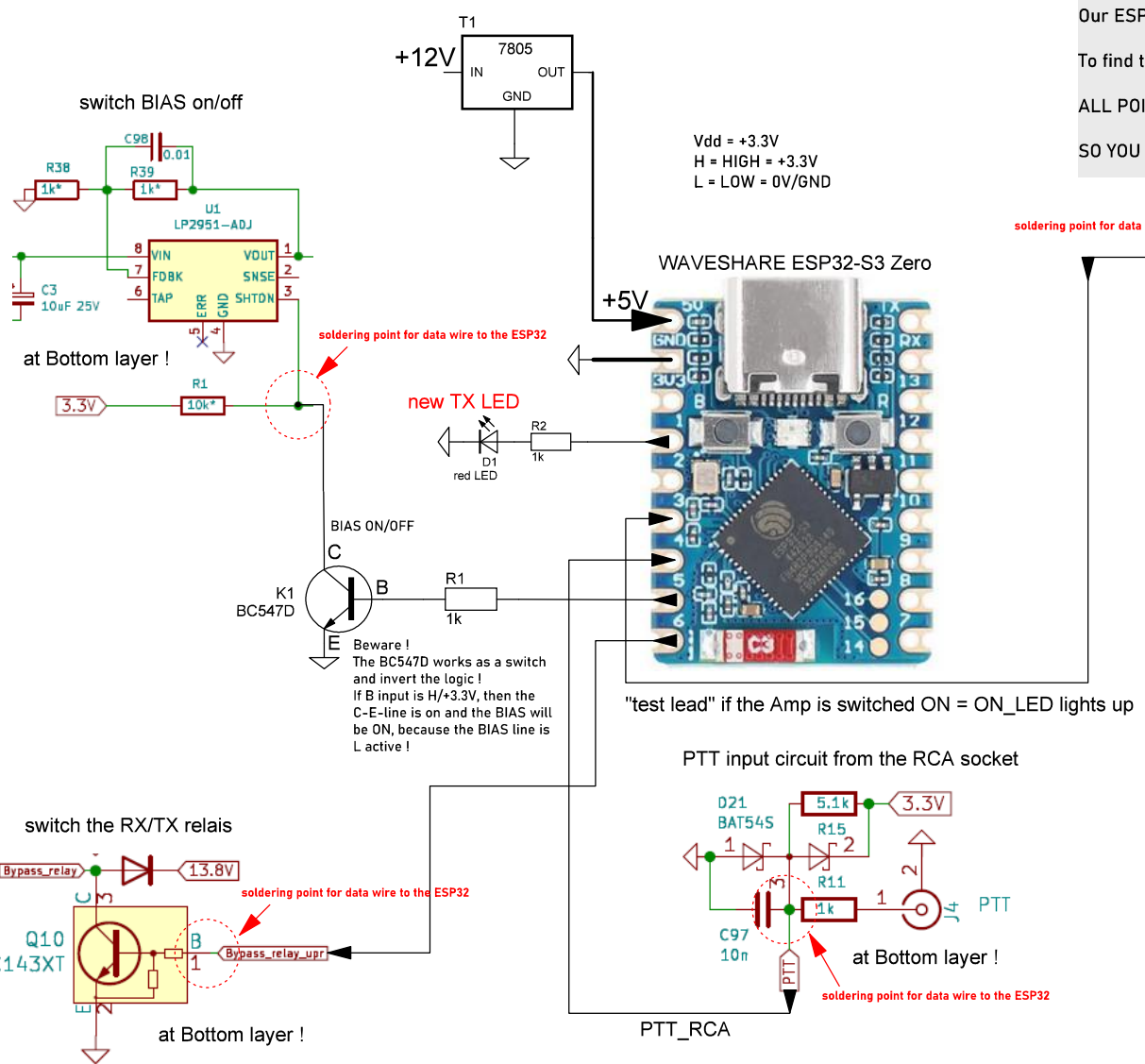


PA switch logics
Signal Transmit Receive

PTT_out (= BIAS on/off)	L	H
Bypass_relay_upr (=RX/TX relays)	H	L
PTT_RCA	L	H




Remark:
We don't touch the build-in SoC STM32.
The automatic band select stay intact through the STM32 !

Our ESP32 starts itself if +12V power supply connected to the amp.

To find the split points for our needed signals you need look into the original schematic of Neptune 50W PA !

ALL POINTS except the TX_LED and ON_LED are located AT THE BOTTOM LAYER !

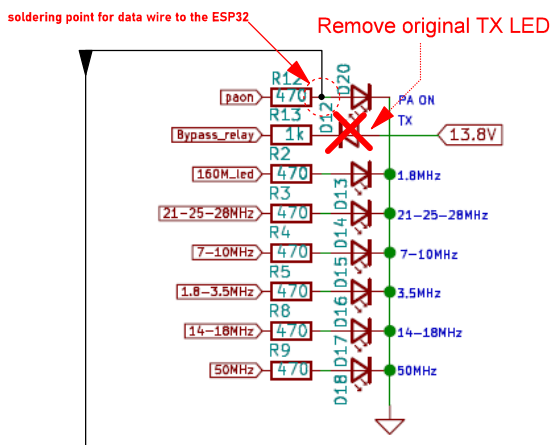SO YOU HAVE TO SCREW OFF THE MAINBOARD FROM HEATSINK for soldering the wires go to the ESP32 !



Replacing amp control Neptune PA 50W with an ESP32 SoC (WAVESHARE ESP32-S3 Zero) especially for stable use with Hermes-Lite 2 idea by DL1BZ & made by DL1BZ in 04/2024

**ONLY for use in Amateur Radio !
NOT for commercial use in any case !
WITHOUT ANY WARRANTY !
YOU DO ALL AT YOUR OWN RISK !**